

Half Bridge Controlled Rectifier using SCR and Arduino

Supriya Mane and G V V Sharma*

CONTENTS

| | | |
|---|-------------------|---|
| 1 | Components | 1 |
| 2 | Circuit Operation | 1 |
| 3 | Working | 1 |
| 4 | Connections | 2 |
| 5 | Calculation | 2 |

Abstract—This manual provides the design of a DC-DC Boost-Converter.

1 COMPONENTS


| Component | Value | Quantity |
|-------------------|--------------|----------|
| Arduino uno | | 1 |
| SCR-2N6509G | | 1 |
| Optocoupler-PC817 | | 2 |
| Diode-IN4007 | | 2 |
| Resistor | 10k Ω | 1 |
| Resistor | 1k Ω | 2 |
| Resistor | 200 Ω | 1 |
| Resistor | 10 W | 1 |
| Potentiometer | 10k Ω | 1 |
| Transformer | 12-0-12 | 1 |
| Breadboard | | 1 |
| Jumper Wire | | 20 |

2 CIRCUIT OPERATION

The SCR (thyristor) is a three-terminal device (Anode, Cathode and Gate) with four layers of

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

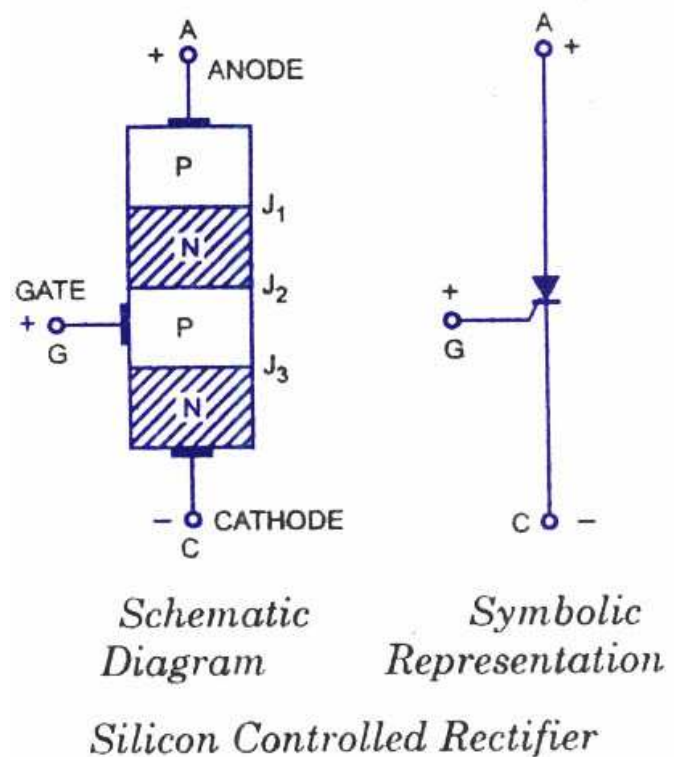alternating p- and n-type material. The gate terminal is used to control the SCR, the anode (A) and cathode (K) are connected in series with the load. The SCR is just a controlled diode. The Thyristor and transistor analogy of SCR is shown in Fig. 1 and Fig. 2.



3 WORKING

In single-phase half-wave rectifier, only one thyristor is used to control the load voltage. The thyristor will conduct (ON state) when the voltage V_t is positive ($V_t > 0$) and a firing current pulse I_g is applied to the gate terminal. Delaying the firing pulse by an angle ' α ' does the control of the load voltage. In the figure below the angle ' α ' is measured from the zero crossing point of the supply voltage V_s .

The load is resistive and therefore current i_d has the

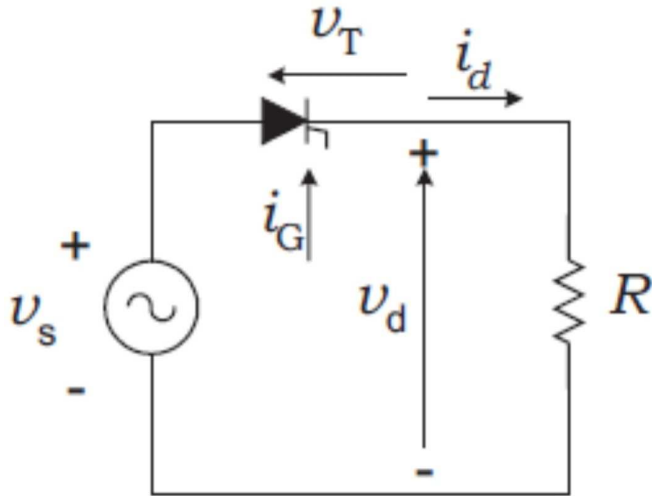


Fig. 1: Operation of Thyristor

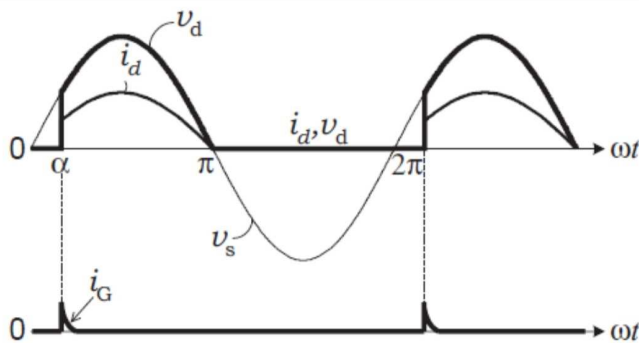


Fig. 2: Transistor Analogy

same waveform as the load voltage. The thyristor goes to the non-conducting condition (OFF state) when the load voltage and, consequently, the current try to reach a negative value.

4 CONNECTIONS

- 1) All grounded terminals are connected together.
- 2) In the circuit there are two optocouplers, optocoupler-1 to detect the zero crossing of the AC voltage signal and optocoupler-2 for firing the SCR.
- 3) The optocouplers are used to isolate the Arduino (control circuit) from the power circuit.
- 4) Diodes D1 and D2 are with the same type (1N4007), D1 is used to protect optocoupler-1 from reverse voltage and D2 to feed the SCR gate with positive current.

- 5) Optocoupler-1 collector pin is connected to Arduino pin 2 which is external interrupt pin, so optocoupler-1 interrupts the Arduino when there is a zero crossing event (when the AC signal goes from positive to negative).
- 6) When the AC voltage is positive, optocoupler-1 is ON and therefore the collector pin is connected to ground.
- 7) Here we used the 10kΩ resistor as pull-up resistor for Arduino pin 2 because we've an open collector output (optocoupler-1).
- 8) The 10k ohm potentiometer is used to control firing angle.
- 9) We got the 12V AC (50Hz) using a step down transformer (220V to 12V).

5 CALCULATION

Let, the input voltage v_i be a sinusoidal voltage of amplitude V_m and frequency f Hz and let be given by,

$$V_i = V_m \sin \omega t = V_m \sin \theta \quad (5.0.1)$$

Where ω is the angular frequency in radians/second and equals $2\pi f$.

Let, α be the firing angle i.e. the angle at which conducting begins. The SCR conducts from α to π radians during the positive half cycle and does not conduct during the negative half cycle.

Then the average output voltage V_{av} is given by,

Eqn. 5.0.2 shows integration

$$V_{av} = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \theta d\theta = \frac{V_m}{2\pi} (1 + \cos \alpha) \quad (5.0.2)$$

Average current is given by:-

$$I_{av} = \frac{V_{av}}{RL} = \frac{V_m}{2\pi RL} (1 + \cos \alpha) \quad (5.0.3)$$

Thus as α increases from 0 to $\frac{\pi}{2}$ radians, $(1 + \cos \alpha)$ reduces and I_{av} reduces. Hence, by varying resistor R , we may control the gate current, control the firing angle and hence control V_{av} and I_{av} .

Problem 5.1. Program the Arduino to generate the output voltage and the zero crossing detector to know the function of SCR.

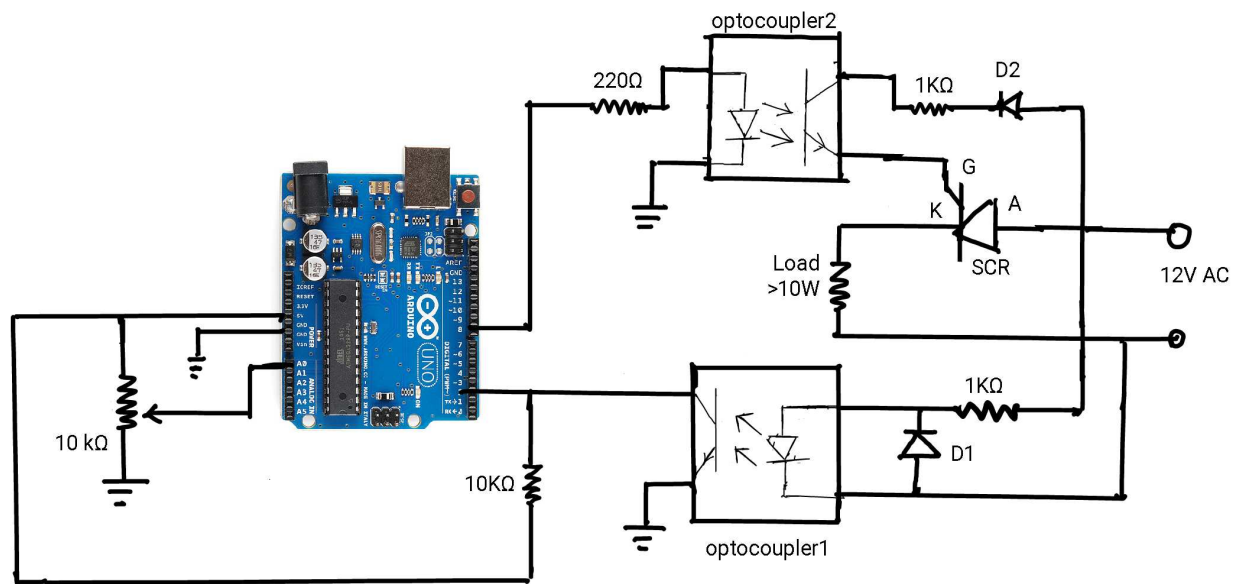


Fig. 3: Circuit Operation