

Butterworth Filter and Sallen-Key Topology

Dheeraj Racha and Utkarsh Bhura *

CONTENTS

1	Introduction	1
2	Frequency Response	1
3	Filter Implementation using Circuits	1
4	Sallen-Key Circuit Analysis	2

Abstract—This manual gives an idea about Butterworth filter and its use in signal processing. Sallen-Key topology is used to implement linear analog filter.

1 INTRODUCTION

1.1 What is a Butterworth Filter?

Solution: It is a low pass filter designed to have a linear magnitude response in pass band. So, it is also referred to as a maximally flat magnitude filter. Even though it does not provide the sharp cut-off response, it is often considered as the all-round filter which is used in many applications.

2 FREQUENCY RESPONSE

2.1 Write a mathematical expression for the magnitude response of this filter.

Solution:

$$|H_n(j\omega)| = \frac{V_o}{V_i} = \frac{1}{\sqrt{1 + (\frac{\omega}{\omega_c})^{2N}}}$$

where ω_c is the cut-off/corner frequency, N is the order of the filter or number of reactive elements in a passive filter.

2.2 Plot the frequency response of an ideal Butterworth filter. Write your inference.

Solution: Refer to Fig.2.2 for frequency response.

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All solutions in this manual is released under GNU GPL. Free and open source.

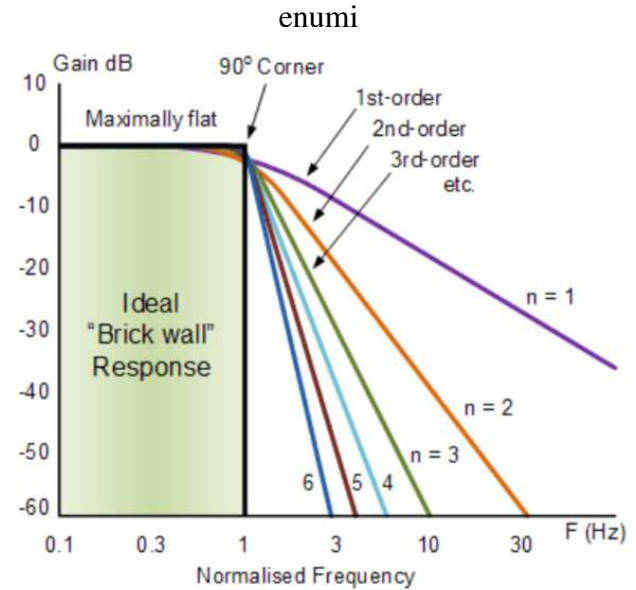


Fig. 2.2

The Butterworth filter achieves pass band flatness at the expense of a wide transition band as the filter changes from the pass band to the stop band.

3 FILTER IMPLEMENTATION USING CIRCUITS

3.1 What are the Filter topologies used to implement this filter.

Solution: There are several different filter topologies available to implement a linear analog filter. The most often used topology for a passive realisation is Cauer topology and the most often used topology for an active realisation is Sallen-Key topology.

3.2 Describe briefly Cauer and Sallen-Key topology.

Solution: (i) *Cauer Topology*: The Cauer topology uses passive components (shunt capacitors and series inductors) to implement a linear analog filter. The Butterworth filter having a given transfer function can be realised

using a Cauer 1-form. Fig shown below is an example of Cauer topology.

(ii) *Sallen-Key Topology*: The Sallen-Key

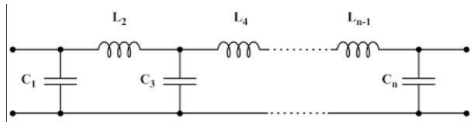


Fig. 3.2

topology uses active and passive components (op-amps operating in non-inverting region, resistors, and capacitors) to implement a linear analog filter. Each Sallen-Key stage implements a conjugate pair of poles; the overall filter is implemented by cascading all stages in series. Fig shown below is an example of Sallen-Key topology.

****NOTE:** We will limit our discussion to

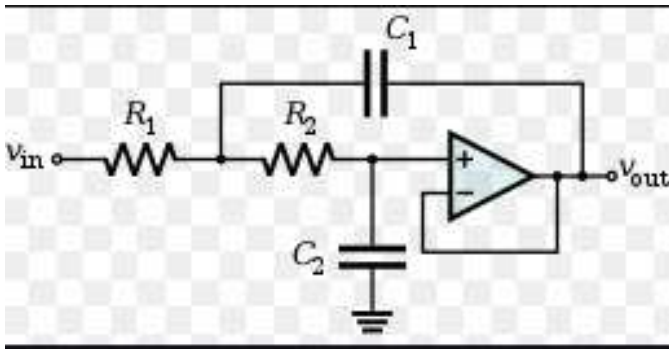


Fig. 3.2: A second order sallen-key filter

Sallen-Key topology only.

4 SALLEN-KEY CIRCUIT ANALYSIS

4.1 Derive the expression for transfer function of a general second order sallen-key filter.

Solution: Because the op-amp is operating in

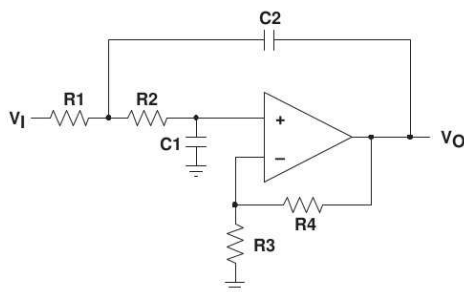


Fig. 4.1

non-inverting region,

$$V_0 = (1 + \frac{R_4}{R_3})V_B \quad (4.1.1)$$

Applying KCL at Node A:

$$\frac{V_A - V_{in}}{R_1} + \frac{V_A - V_B}{R_2} + \frac{V_A - V_{out}}{1/C_2 s} = 0 \quad (4.1.2)$$

$$\text{Similarly at Node B: } \frac{V_B - V_A}{R_2} + \frac{V_B}{1/C_1 s} = 0$$

$$\Rightarrow V_A = (1 + R_2 C_2 s) V_B \quad (4.1.3)$$

Also,

$$k = \frac{R_3 + R_4}{R_3} \quad (4.1.4)$$

On solving the above equations for $\frac{V_o}{V_i}$, we have,

$$\frac{V_o}{V_i} = \frac{\frac{k}{R_1 R_2 C_1 C_2}}{s^2 + s \frac{R_1 C_2 + R_2 C_2 + R_1 C_1 (1 - k)}{R_1 R_2 C_1 C_2} + \frac{1}{R_1 R_2 C_1 C_2}} \quad (4.1.5)$$

4.2 Design a general 2nd order butterworth low pass filter with cut-off frequency f_c Hz .

Solution: $\omega_c = 2\pi f_c$

$$\text{In (4.1.5), } Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{R_1 C_2 + R_2 C_2 + R_1 C_1 (1 - k)}$$

$$\omega_c = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}. \text{ And } K = 3 - \frac{1}{Q} = 1 + \frac{R_4}{R_3}.$$

Let $R_1 = R_2 = R$ and $C_1 = C_2 = C$. And for Butterworth Filter $Q = 0.707$.

$$\text{Therefore } H(s) = \frac{1.586 \omega_c^2}{s^2 + 1.414 \omega_c s + \omega_c^2}$$

$$\text{and } R_4 = 0.586 R_3$$

4.3 Design a 4th order Butterworth filter with cut-off frequency 1 kHz.

Solution: Cascading two 2nd order butterworth filters realised with sallen-key topology

we get,

$$\omega_c = 2000\pi \text{ rad/sec}$$

$$H(S) = \frac{2.57 \omega_c^4}{(s^2 + 0.7654 \omega_c s + \omega_c^2)(s^2 + 1.8478 \omega_c s + \omega_c^2)}$$